

Alarm Clock Circuit Diagram

Catherine Baker | May 1, 2023

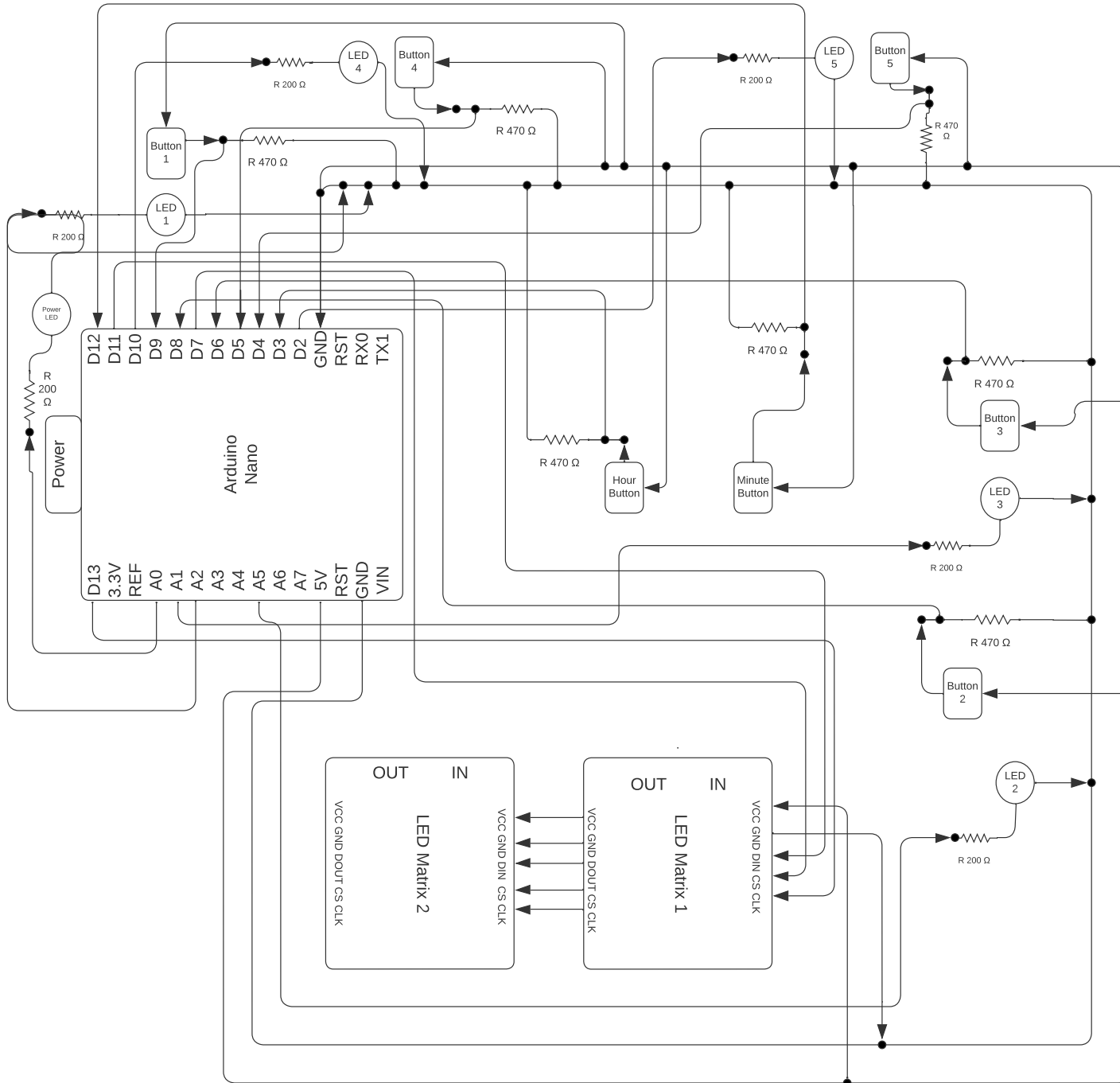


Diagram Key

- LED
- Button or Matrix
- Wire
- ⏏ Resistor
- Connected Wires
- + Unconnected wires that share space